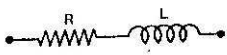
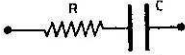
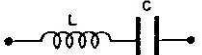
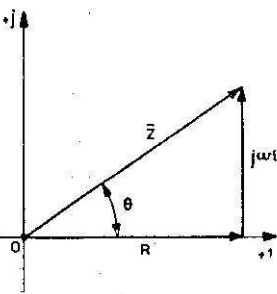
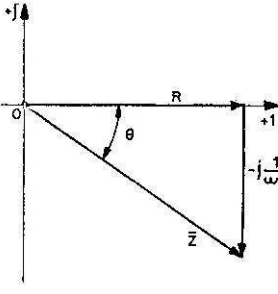
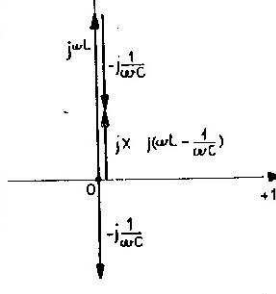


TABELLA 5.54

Impedenza			
Forma binomia	$R + j \omega L$ $R + j X_L$	$R - j \frac{1}{\omega C}$ $R - j X_C$	$0 + j \left(\omega L - \frac{1}{\omega C} \right)$ $0 + j X$
Rappresentazione nel piano complesso			
Modulo	$\sqrt{R^2 + (\omega L)^2}$	$\sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}$	$\omega L - \frac{1}{\omega C}$
Argomento	$tg \theta = \frac{\omega L}{R}$	$tg \theta = -\frac{1}{R} = -\frac{1}{\omega C R}$	$tg \theta = \frac{\omega L - \frac{1}{\omega C}}{R} = \pm \infty$ $\theta = \pm \pi/2$
Valore istantaneo corrente [riferito alla tensione $E_M \text{ sen}(\omega t + \xi)$]	ritardo ($\varphi < 0$) $i = \frac{E_M}{\sqrt{R^2 + (\omega L)^2}} \text{ sen}(\omega t + \xi + \varphi)$	anticipo ($\varphi > 0$) $i = \frac{E_M}{\sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}} \text{ sen}(\omega t + \xi + \varphi)$	quadratura $i = \frac{E_M}{\omega L - \frac{1}{\omega C}} \text{ sen}(\omega t + \xi + \varphi)$
Valore efficace corrente	$I = \frac{E}{\sqrt{R^2 + (\omega L)^2}}$	$I = \frac{E}{\sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}}$	$I = \frac{E}{\omega L - \frac{1}{\omega C}}$
Sfasamento φ	$\varphi = -\theta$	$\varphi = -\theta$	$\varphi = -\theta$